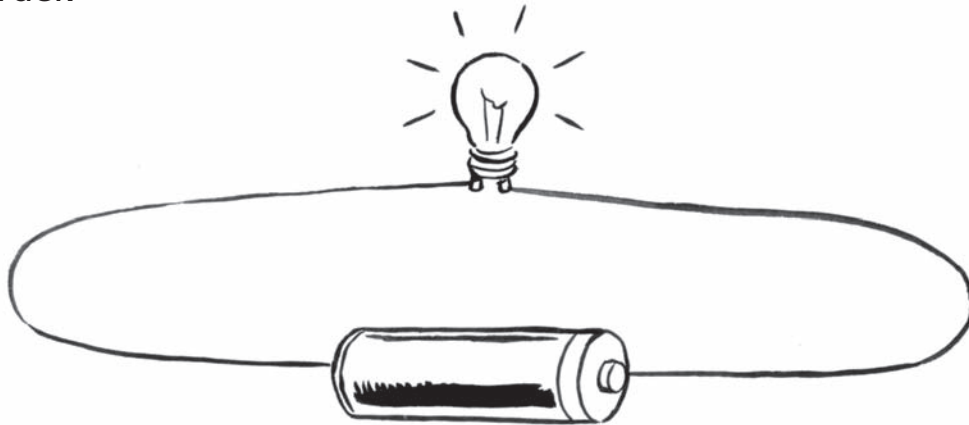


Name

Date

How I made a bulb light up

- The statements explaining how someone made a bulb light up are in the wrong order.
- Cut them out and stick them onto another piece of paper in the right order.



<p>Next I connected the other ends of the wires to each end of the battery to make a complete circuit.</p>	<p>A circuit is like a ring of metal for electricity to flow around.</p>
<p>I am going to explain how I made the bulb light up.</p>	<p>A break in the circuit would stop the flow of electricity.</p>
<p>When I had made a complete circuit by attaching the wires to the bulb and the battery, the bulb lit up.</p>	<p>Firstly I connected the wires to the metal part of the bulb.</p>

Dear helper

Objective: To understand how to explain a process.

Task: Support your child in sorting out the order of the explanation of how to make a bulb light up. Talk about the words that link together why and how as these give clues as to the correct order of the process.