
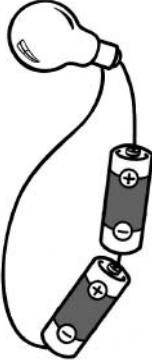





# Testing circuits

Circuit	Prediction Will it work? Yes/No	Result Did it work? Yes/No	Explanation Why did this happen?
			
			
			
			
			

Illustrations © Mark Brierley / Beehive Illustration